
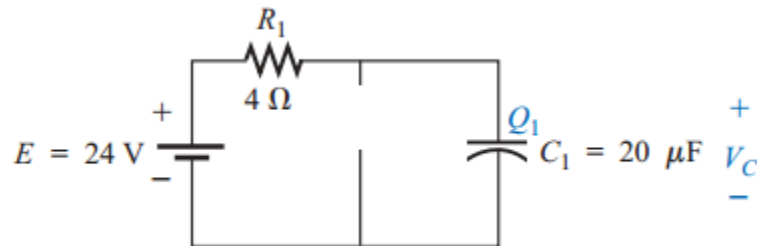


Consider the following Circuit

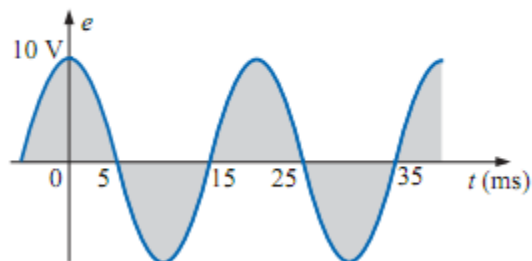


1. A) How much time does it take to get fully charged?
 B) Energy stored by the capacitor $C_1 = ?$

Consider the following figure.




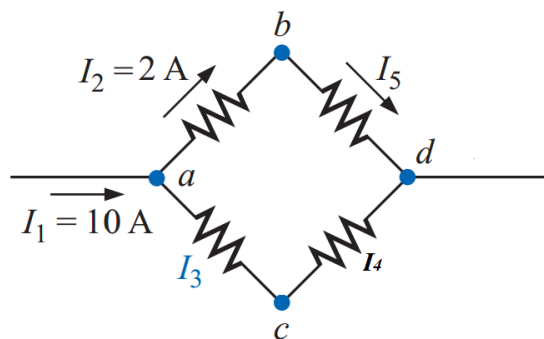2. A) Write the equation for voltage for the sinusoidal wave above.
 B) Determine frequency.
 C) Find Equivalent DC voltage $E_{\text{eff.}}$.
3. Find I_3 , I_4 and I_5 from the following




4. You have four capacitors of $10\mu\text{F}$. Can you make $25\mu\text{F}$ using these? Draw the circuit.
5. Write short note
 - I. Norton Theorem.
 - II. Thevenin Theorem

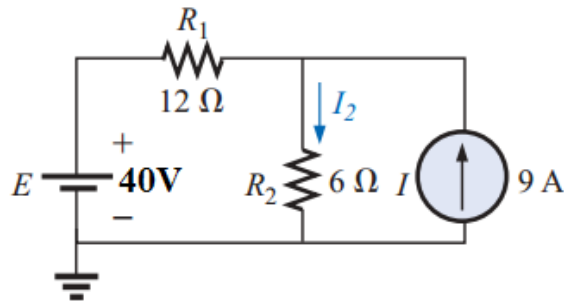
6. Apply superposition theorem and find current I_2 from the circuit below.



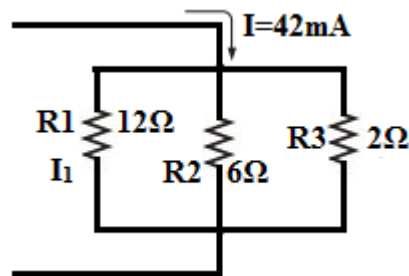- 7.
- Write difference between DC and AC.
 - Calculate power factor where $v = 120 \sin(\omega t + 80^\circ)$ and $i = 5 \sin(\omega t + 30^\circ)$
8. Calculate I_1 from the following



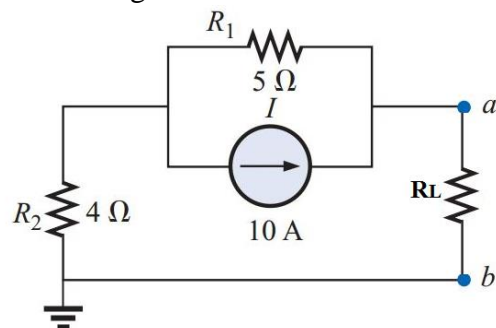9. Find Norton equivalent of the following circuit.



10. What is the condition for a load to receive maximum power? Calculate maximum power for R_L in the following circuit.

